


✓
Congratulations! You passed!
Keep Learning
GRADE 90%

Module 7 Quiz

LATEST SUBMISSION GRADE
 90%

1. What is the equivalent inductance for the following circuit if $L_1 = L_2 = L_3 = L_4 = 5mH$? Give your answer in mH, without entering the units.

1 / 1 point

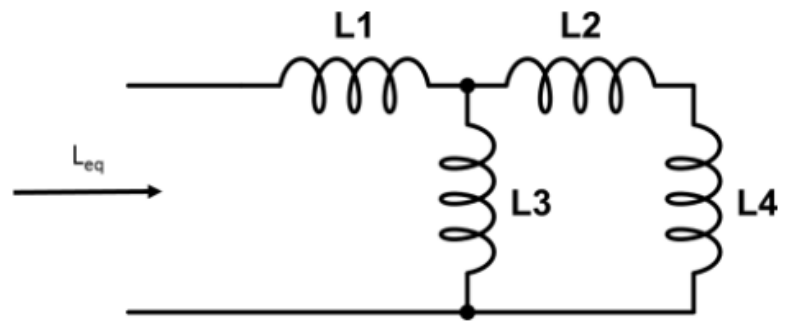

8.33


✓ Correct

2. What is the equivalent capacitance for the following circuit if $C_1 = C_2 = C_3 = 10pF$? Give your answer in pF, without entering the units.

1 / 1 point

2. What is the equivalent capacitance for the following circuit if $C_1 = C_2 = C_3 = 10\text{pF}$? Give your answer in pF, without entering the units.

1 / 1 point

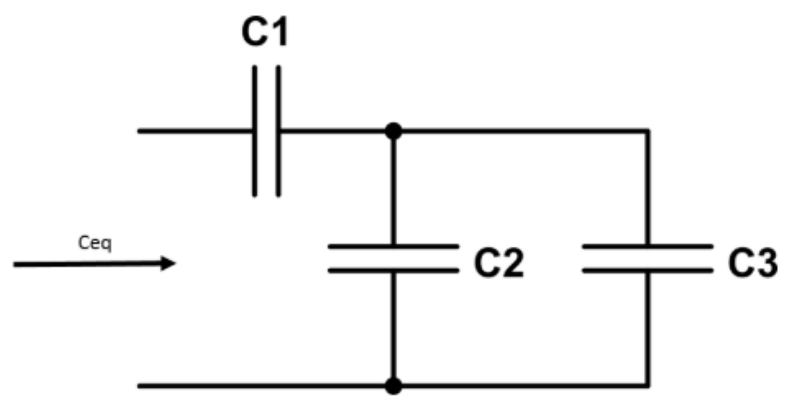


6.66

✓ Correct


3. Use the following circuit for this problem. Let $R = 1000\Omega$, $C = 100\mu\text{f}$, $V_c(0) = 0\text{V}$ and $V_s = 10\text{V}$

1 / 1 point

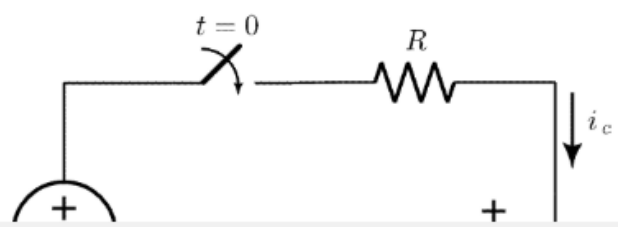

3. Use the following circuit for this problem. Let $R = 1000\Omega$, $C = 100\mu f$, $V_c(0) = 0V$ and $V_s = 10V$

1 / 1 point

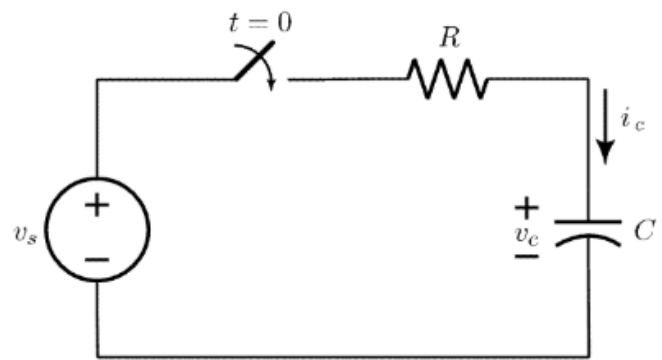

What is the initial value of $V_c(t)$ just prior to the switch closing? Assume that the circuit had reached a steady-state value prior to the switch opening. Enter your answer in the box below without unit.

✓ Correct


4. What is $V_c(t)$ at $t = 5$ seconds if $I_s = 4mA$, $C = 20mF$ and $V_c(0) = 0V$? Give your answer in V, without entering the units.

1 / 1 point



4. What is $V_C(t)$ at $t = 5$ seconds if $I_s = 4mA$, $C = 20mF$ and $V_C(0) = 0V$? Give your answer in V, without entering the units.

1 / 1 point

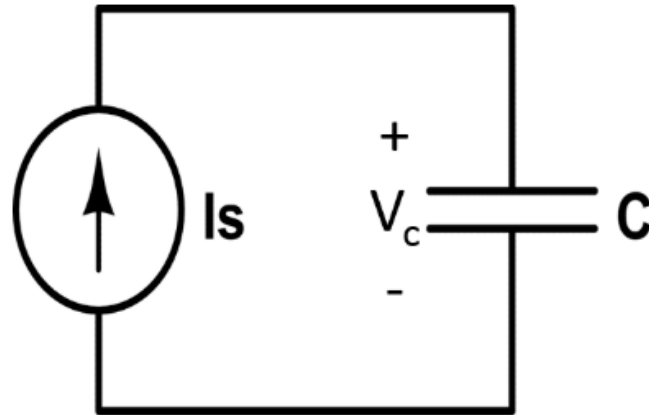

1

✓ Correct


5. What is $V_L(t)$ at $t = 5$ seconds if $I_s = -t^2 A$ and $L = 2mH$? Give your answer in mV, without entering the units.

1 / 1 point



5. What is $V_L(t)$ at $t = 5$ seconds if $I_s = -t^2 A$ and $L = 2mH$? Give your answer in mV, without entering the units.

1 / 1 point

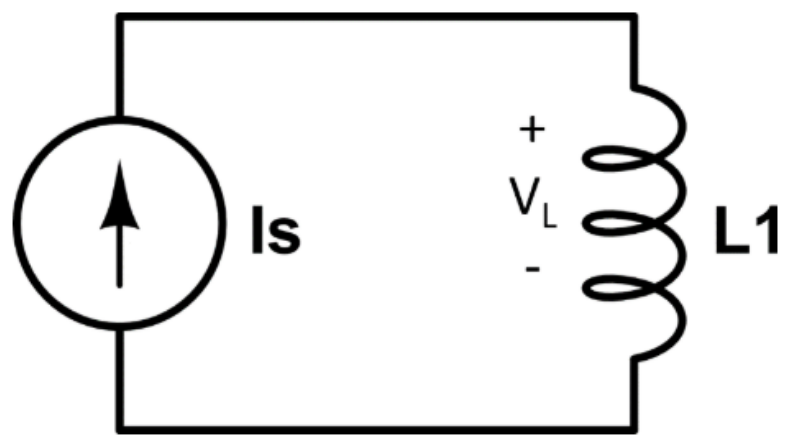


-20

✓ Correct


6. In the circuit below, the switch is closed for a long time before time $t = 0$. $V_s = 24V$, $R_1 = 300\Omega$, $C_1 = 10\mu F$ and $C_2 = 20\mu F$.

1 / 1 point

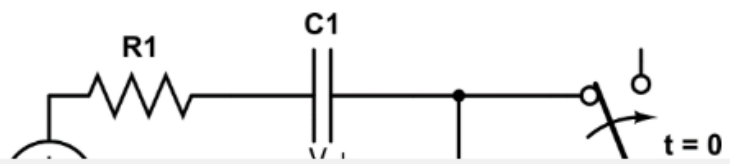

6. In the circuit below, the switch is closed for a long time before time $t = 0$.
 $V_s = 24V$, $R_1 = 300\Omega$, $C_1 = 10\mu F$ and $C_2 = 20\mu F$.

1 / 1 point

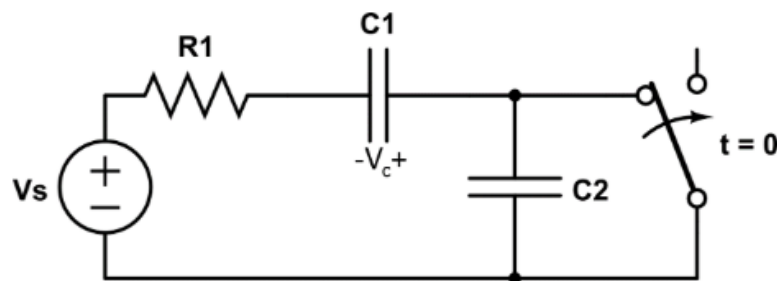

What is the voltage V_c across capacitor C_1 when the switch is closed? Give your answer in V, without entering the units.

-24



Correct


7. Suppose you have the following circuit. The switch has been open for a long time, and is closed at time $t = 0$.

0 / 1 point

Assume $V_2 = 5V$, $R_2 = 10k\Omega$, $L_2 = 2mH$, $C_2 = 0.1\mu F$

The second order differential equation for the voltage across the capacitor is
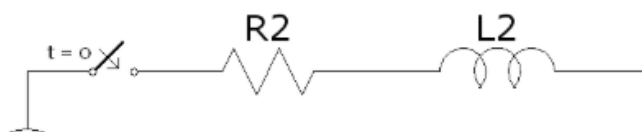
$$d^2 V_c(t)/dt + a_1 dV_c(t)/dt + a_2 V_c = K$$




7. Suppose you have the following circuit. The switch has been open for a long time, and is closed at time $t = 0$.

0 / 1 point

Assume $V_2 = 5V$, $R_2 = 10k\Omega$, $L_2 = 2mH$, $C_2 = 0.1\mu F$

The second order differential equation for the voltage across the capacitor is
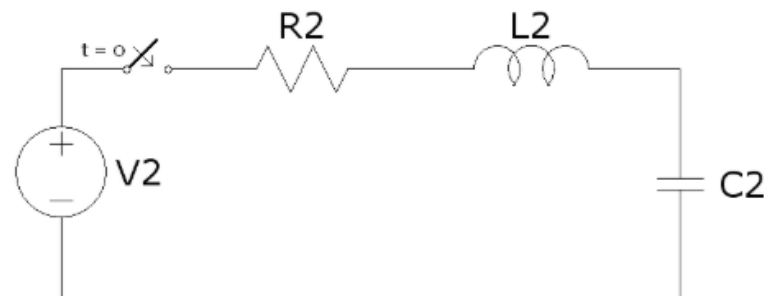
$$d^2 V_c(t)/dt + a_1 dV_c(t)/dt + a_2 V_c = K$$



What is the coefficient K of the 2nd order differential equation for this circuit? Do not use scientific notation.

10

Incorrect

8. By rotating the dial of an antenna tuner, what are we manipulating within the circuit element?

1 / 1 point

☐ Resistance

☒ Capacitance

8. By rotating the dial of an antenna tuner, what are we manipulating within the circuit element?

1 / 1 point

☐ Resistance


☒ Capacitance

✓ Correct

☐ Inductance

9. Suppose the following voltage is applied across the terminals of a $1\mu\text{F}$ capacitor.

1 / 1 point

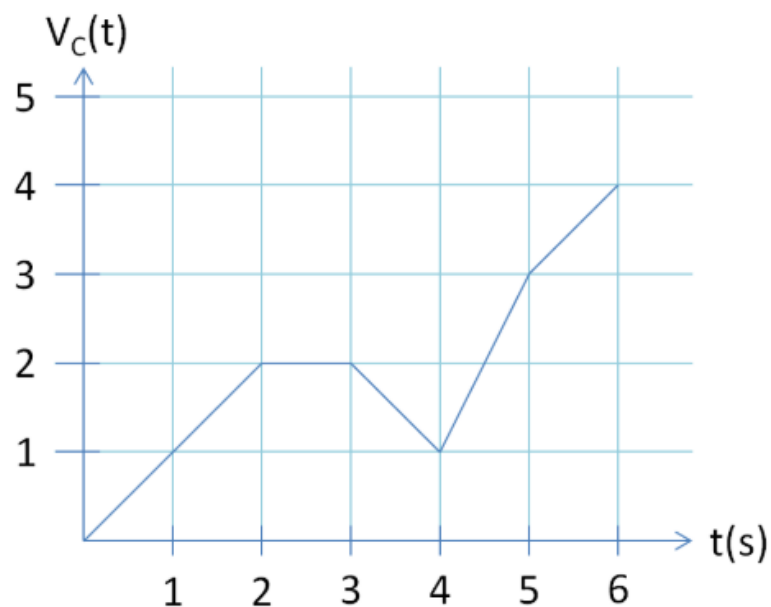




What is the current through the capacitor at time $t = 4.5$ sec? Give your answer in μA , without entering the units.

2

✓ Correct

10. An RC circuit has the following response. The units on the time axis are in seconds, but note the scaling of 10^{-3} on the axis (so the first tick mark is 0.5 milliseconds). Determine the time constant, in milliseconds, and enter that value in the box below without the units.

1 / 1 point

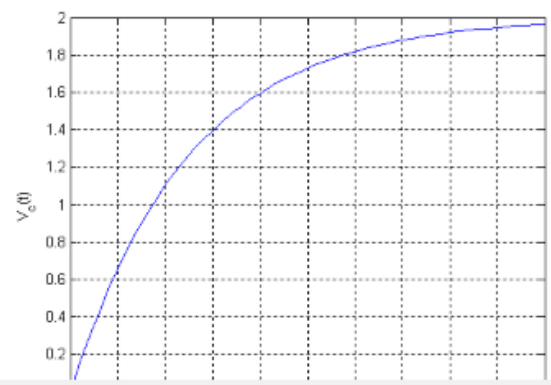


2

✓ Correct

10. An RC circuit has the following response. The units on the time axis are in seconds, but note the scaling of 10^{-3} on the axis (so the first tick mark is 0.5 milliseconds). Determine the time constant, in milliseconds, and enter that value in the box below without the units.

1 / 1 point

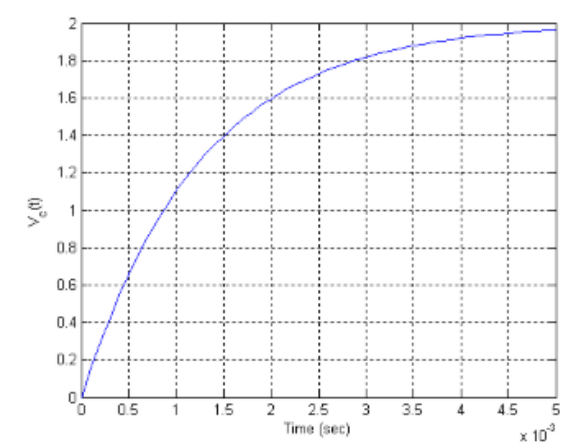

1.264

✓ Correct