

✓ **Congratulations! You passed!**  
TO PASS 70% or higher

Keep Learning

GRADE  
100%


## Module 5 Quiz

LATEST SUBMISSION GRADE

100%

1. What is the equivalent inductance for the following circuit if  $L_1 = L_2 = L_3 = L_4 = 5\text{mH}$ ? Give your answer in mH, without entering the units.

1 / 1 point

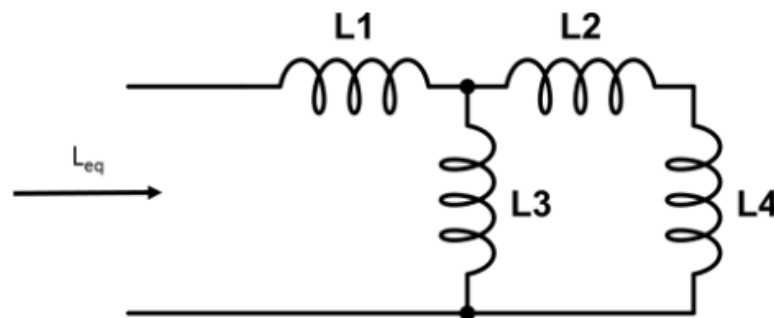

8.33

✓ Correct


2. What is the equivalent capacitance for the following circuit if  $C_1 = C_2 = C_3 = 10\text{pF}$ ? Give your answer in pF, without entering the units.

1 / 1 point

C1

2. What is the equivalent capacitance for the following circuit if  $C_1 = C_2 = C_3 = 10\text{pF}$ ? Give your answer in  $\text{pF}$ , without entering the units.

1 / 1 point

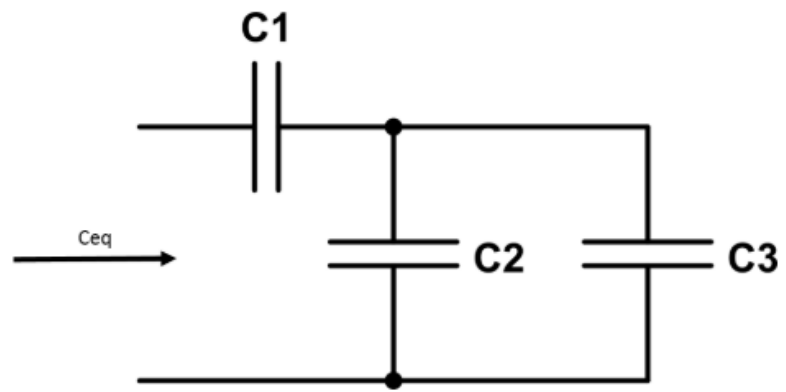


6.66

✓ Correct


3. What is  $V_c(t)$  at  $t = 5$  seconds if  $I_s = 4\text{mA}$ ,  $C = 20\text{mF}$  and  $V_c(0) = 0\text{V}$ ? Give your answer in V, without entering the units.

1 / 1 point

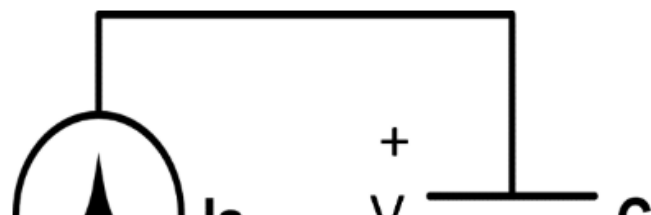

3. What is  $V_C(t)$  at  $t = 5$  seconds if  $I_s = 4mA$ ,  $C = 20mF$  and  $V_C(0) = 0V$ ? Give your answer in V, without entering the units.

1 / 1 point

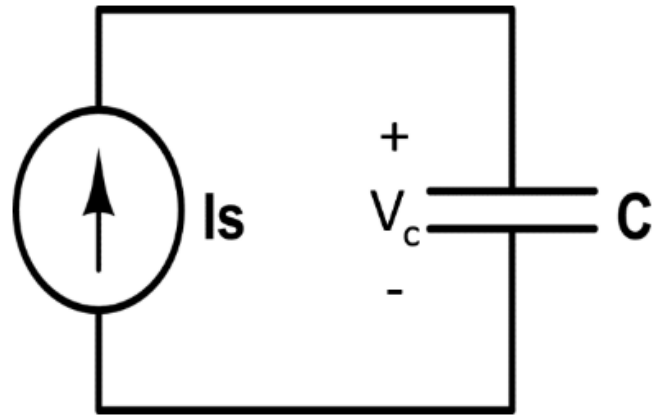

1

✓ Correct


4. What is  $V_L(t)$  at  $t = 5$  seconds if  $I_s = -t^2 A$  and  $L = 2mH$ ? Give your answer in mV, without entering the units.

1 / 1 point



4. What is  $V_L(t)$  at  $t = 5$  seconds if  $I_s = -t^2 A$  and  $L = 2mH$ ? Give your answer in mV, without entering the units.

1 / 1 point

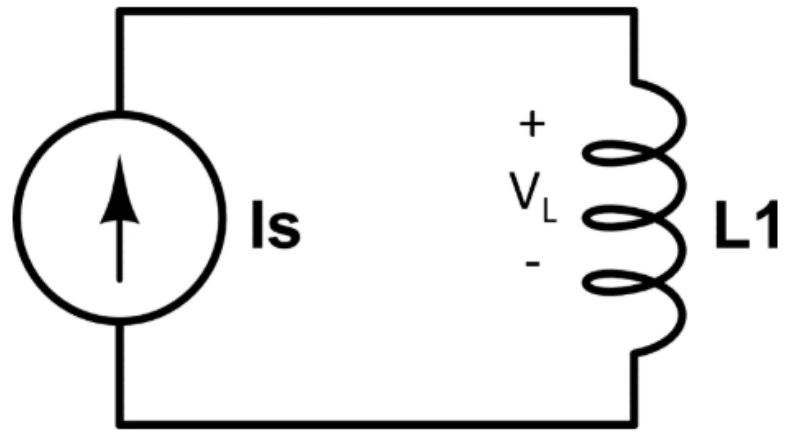

-20

✓ Correct


5. Suppose the following voltage is applied across the terminals of a  $5\mu F$  capacitor. What is the current through the capacitor at time  $t = 5$  sec? Give your answer in  $\mu A$ , without entering the units.

1 / 1 point



5. Suppose the following voltage is applied across the terminals of a  $5\mu F$  capacitor. What is the current through the capacitor at time  $t = 5$  sec? Give your answer in  $\mu A$ , without entering the units.

1 / 1 point

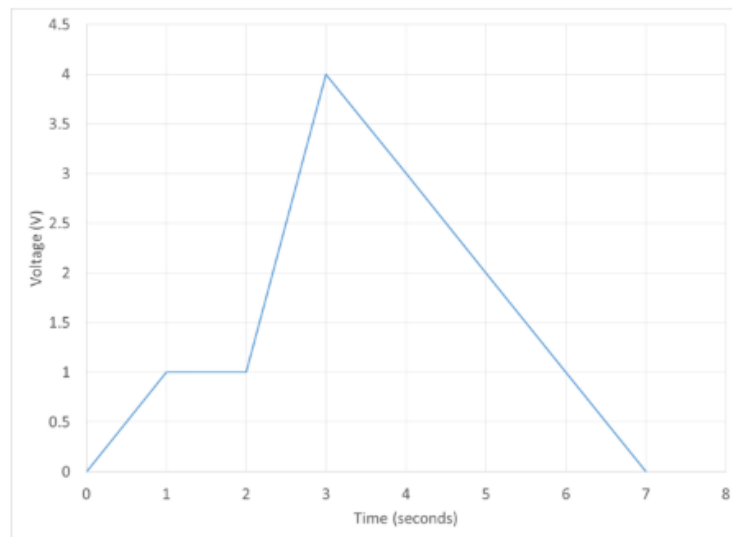

-5

✓ Correct

6. Suppose that a  $10mF$  capacitor has a constant current of  $i(t) = 2mA$  flowing through it.

1 / 1 point

Assuming the capacitor starts with no initial voltage across it,  $V_c(0) = 0$ , what is the the voltage across the capacitor at  $t=6$  seconds?

☐ 0.012V

6. Suppose that a 10mF capacitor has a constant current of  $i(t) = 2\text{mA}$  flowing through it.

1 / 1 point


Assuming the capacitor starts with no initial voltage across it,  $V_c(0) = 0$ , what is the the voltage across the capacitor at  $t=6$  seconds?

- ☐ 0.012V
- ☒ 1.2V
- ☐ 0V
- ☐ -5V

✓ Correct

7. What is the equivalent inductance for the following circuit if  $L_1 = 10\text{mH}$ ,  $L_2 = 20\text{mH}$ ,  $L_3 = 20\text{mH}$ ?

1 / 1 point

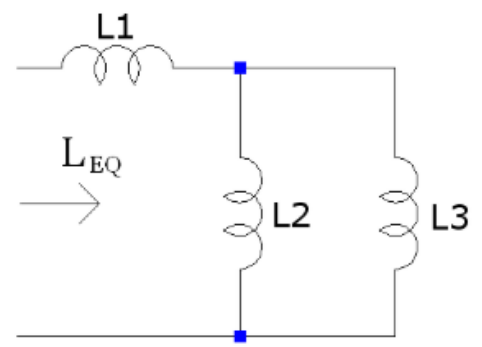


Give your answer in mH, without entering the units.

✓ Correct

8. What is the equivalent capacitance for the following circuit if  $C_1 = 5\text{pF}$ ,  $C_2 = 10\text{pF}$ ,  $C_3 = 20\text{pF}$ ,  $C_4 = 20\text{pF}$ ?

1 / 1 point

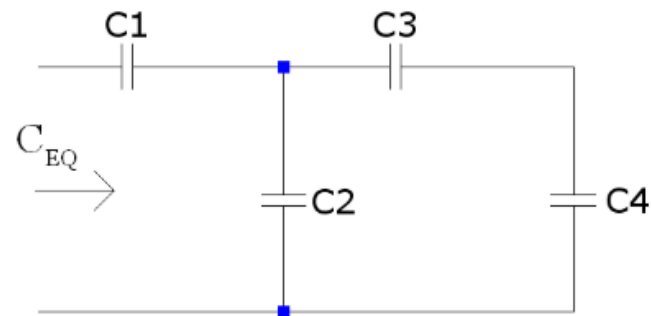

Give your answer in pF, without entering the units.

4

✓ Correct


9. Suppose the following voltage is applied across the terminals of a  $1\mu\text{F}$  capacitor.

1 / 1 point



9. Suppose the following voltage is applied across the terminals of a  $1\mu F$  capacitor.

1 / 1 point

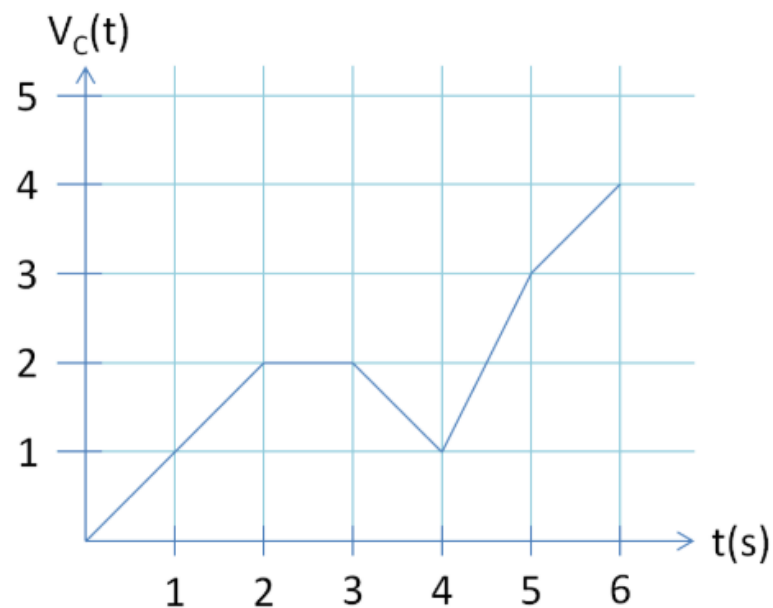

What is the current through the capacitor at time  $t = 4.5$  sec? Give your answer in  $\mu A$ , without entering the units.


2

✓ Correct



10. Consider the following circuit composed of two capacitors,  $C_1 = 5\mu F$  and  $C_2 = 3\mu F$ , in parallel with a constant  $12V$  DC source.

1 / 1 point

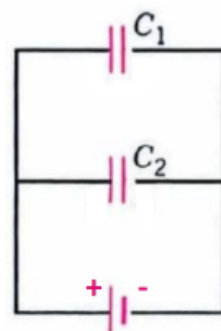

Find the voltages  $V_1$  and  $V_2$  across each of the capacitors  $C_1$  and  $C_2$  respectively.

Enter the value of  $V_1$  below in Volts.

12

✓ Correct

11. Enter the value of  $V_2$  below in Volts.

1 / 1 point

12

✓ Correct

12. Find the charges  $q_1$  and  $q_2$  of  $C_1$  and  $C_2$  respectively.

1 / 1 point

Enter the value of  $q_1$  below in  $\mu C$ .

60

✓ Correct

13. Enter the value of  $q_2$  below in  $\mu C$ .

1 / 1 point

36

✓ Correct

14. Find the energies  $W_1$  and  $W_2$  stored in the capacitors  $C_1$  and  $C_2$  respectively.

1 / 1 point

Enter the value of  $W_1$  below in  $\mu J$ .

360

✓ Correct

15. Enter the value of  $W_2$  below in  $\mu J$ .

1 / 1 point

216

✓ Correct